

Q1) a- What is the meaning of single ended signal, differential signal and give example.

b- What is sample and what is hold and when we use them.

[6 pts]

2.39

Q2) Using Temperature sensor (RTD-PT100), in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R_1=110$, $R_2=120$), and using voltage to frequency converter VFC (scale factor = $10KHz/1.12V$).

a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.

b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is ~~100C~~ $55^{\circ}C$.

c- Draw Block diagram of the circuit.

[16 pts]

Q3) An accelerometer sensor sensitivity is $0.145mA/g$, used for measuring pressure in the range ($\pm 20 g$). and the value of its output @ $0 g$ is $5.2mA$, using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

a) Calculate sensor output range (current, voltage, Binary).

$$= \frac{I_{\text{input}} + V_{\text{ref}}}{R_V}$$

b) What is the digital output of ADC at the acceleration is $8 g$.

c) What is the value of acceleration when the digital output is $0DH, 92H$.

[15 pts]

d) If the frequency of the signal is $120Hz$ and there is unwanted noise with frequency $15KHz$, design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range.

[05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at $12.4^{\circ}C$.

Temperature ($^{\circ}C$)	0	5	10	15	20
Resistance (Ω)	102.6	105.1	106.3	107.1	108.3

190

103.6

105.1

106.3

107.1

108.3

[08 pts]



Good Luck (Zeyad)

Q2) RTD-PT 100 , (30°~90° c), wheatstone bridge ($V_s=9V$, $R_1=110\Omega$, $R_2=120\Omega$)
VFC (10 KHZ / 1.12V)

$$\left((30 \times 0.39) + 100 \sim (90 \times 0.39 \frac{\Omega}{^\circ C}) + 100 \right) \Rightarrow (111.7 \Omega \sim 135.1) \text{ Sensor o/p}$$

$$R_1 R_4 = R_2 R_3 \Rightarrow 110 * 111.7 = 120 * R_3 \Rightarrow R_3 = 102.39$$

$$V_a = 9 \times \frac{102.39}{102.39 + 110} = 4.339 V, V_{b1} = 9 \times \frac{111.7 \Omega}{111.7 + 120} = 4.339$$

$$V_{b2} = 9 \times \frac{135.1}{135.1 + 120} = 4.766 V, V_{b1} - V_a = 0 V, V_{b2} - V_a = 0.427 V$$

- Wheatstone bridge o/p Range (0 ~ 0.427 V)

- VFC o/p Range (0 ~ 3.8125 KHZ)


- Counter o/p " ($\frac{1}{180}$ sec) \Rightarrow (0 ~ 21.18 Pulse)

b) $T=55^\circ \rightarrow$ Counter o/p \Rightarrow !?

$$(55 \times 0.39) + 100 = 121.45 \Omega \Rightarrow V_b = 9 \times \frac{121.45}{121.45 + 120} = 4.527$$

$$V_b - V_a = 0.188 V \Rightarrow 0.188 \times \frac{10 KHZ}{1.12 V} = 1.678 KHZ$$
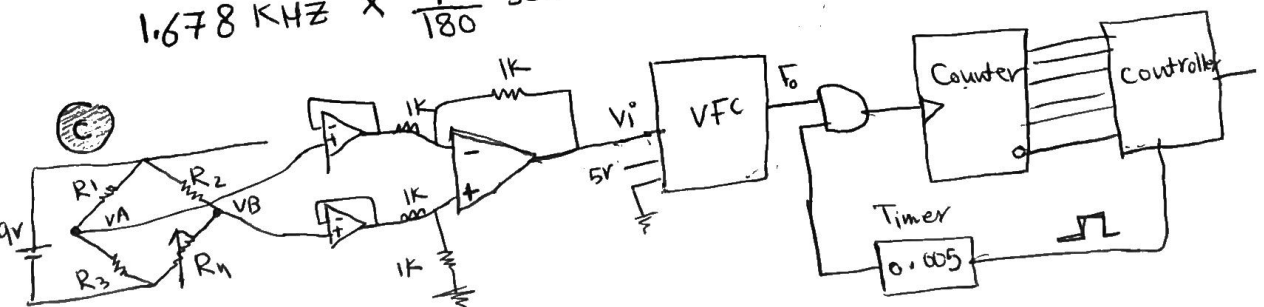
$$1.678 KHZ \times \frac{1}{180} \text{ sec} = 9.32 \text{ Pulse \#}$$



Q(3) 0.14 mA/g ($\pm 20\text{g}$) @ $0\text{g} = 5.2 \text{ mA}$
 $R = 190 \Omega$ (8 bit) ADC $\pm 4 \text{ V}$ reference

$$((-20 \times 0.14) + 5.2) \sim ((20 \times 0.14) + 5.2) \Rightarrow (2.4 \sim 8 \text{ mA}) \text{ sensor o/p}$$

$$(0.456 \text{ V} \sim 1.52 \text{ V}) \text{ Range in Volt}, (142 \sim 176) \text{ Digital o/p}$$

$$\Delta = \frac{8}{2^8} = 0.03125, \text{ Digital o/p} = \frac{\text{analog I/P} + 4}{\Delta \text{V}}$$

$$(1000110 \sim 10110000) \text{ o/p Range in binary}$$

Δ Digital o/p for 8g

$$(8 \times 0.14) + 5.2 = 6.32 \text{ mA} \rightarrow 6.32 \times 190 = 1.2 \text{ V}$$

$$(1.2 + 4) / 0.03125 = 166 \rightarrow (10100110)_2$$

Δ acceleration value if a/p (0D, 92)

$$\text{analog I/P} = -3.594 \text{ V}, 0.5625 \text{ V}$$

$$\text{in mA} = \text{out of Range}, 2.9 \text{ mA}$$

$$\text{acceleration} = , -16.42 \text{ g}$$

$$(00001101)_2, (10010010)_2$$

$$\Downarrow \quad \Downarrow$$

$$(13)_{10} \quad (146)_{10}$$

Δ $F_s = 120 \text{ Hz}$, $F_N = 15 \text{ KHz}$, attenuate Noise 18%.

$$18\% = \frac{1}{\sqrt{1 + \left(\frac{15 \text{ KHz}}{F_c}\right)^2}} \Rightarrow F_c = 2745 \text{ Hz}$$

$$\text{effect on The o/p} = \frac{1}{\sqrt{1 + \left(\frac{120}{2745}\right)^2}} = 99.9\% \quad \text{very Good}$$

"Low Pass Filter"

Q(4)

$^{\circ}\text{C}$	0	5	10	15	20
R	103.6	105.1	106.3	107.1	108.3
	①		⑥		②

$$T_m = 12.4^{\circ}\text{C}$$

$$R(T) = R(T_0) (1 + \alpha \Delta T + \alpha_2 \Delta T^2)$$

$$108.3 = (106.3) (1 + 2.211 \times 10^{-3} (10) + \alpha_2 (10)^2)$$

$$\alpha_2 = -3.295 \times 10^{-5}$$

$$\begin{aligned} \alpha &= \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1} \\ &= \frac{1}{106.3} \times \frac{108.3 - 103.6}{20 - 0} \\ &= 2.211 \times 10^{-3} \end{aligned}$$

$$T = 12.4^{\circ}\text{C} \rightarrow \Delta T = 2.4$$

$$R(T) = 106.3 (1 + 2.211 \times 10^{-3} \times 2.4 + 3.295 \times 10^{-5} \times (2.4)^2)$$

$$R(T) = 106.84 \Omega$$

Final Fall - 2018

Q(1) RTD-PT100 ($22 \sim 190^{\circ}\text{C}$) \rightarrow (0~3V), ADC, Voltage Divider
 $V_s = 9\text{V}$, $R_1 = 200$

$$\triangleleft ((22 \times 0.39) + 100) \sim ((190 \times 0.39) + 100) \Rightarrow (108.58 \sim 174.1 \Omega)$$

$$V_1 = 9 \times \frac{108.58}{108.58 + 200} = 3.16, V_2 = 9 \times \frac{174.1}{174.1 + 200} = 4.18, (3.16 \sim 4.18 \text{ V})$$

$$0 = 3.16 \text{ M} + \text{offset}$$

$$3 = 4.18 \text{ M} + \text{offset}$$

$$3 = 1.02 \text{ M}$$

$$M = 2.94$$

$$\text{offset} = -9.29$$

$$[V_0 = 2.94 \text{ V} - 9.29]$$

$$\frac{102}{1018}$$

$$\Delta V = \frac{3}{2^8} = 0.0117$$


$$\text{Digital o/p} = \frac{\text{analog I/P}}{0.0117}$$

$$(255)_{10}$$

$$(4095)_{16}$$

$$(0 \sim 256)_{10}$$

3

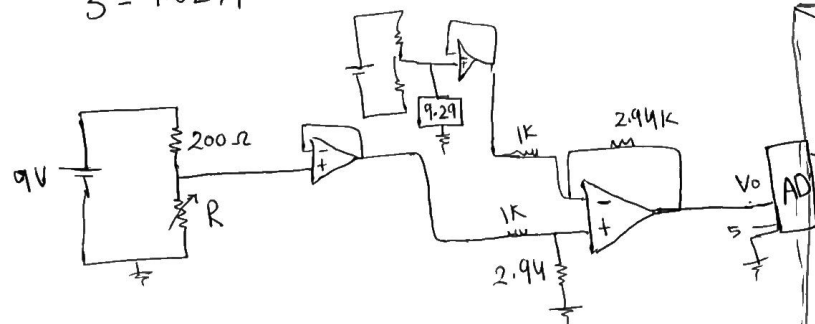

$\triangle 100^{\circ}\text{C}$

$$(100 \times 0.39) + 100 = 139 \Omega \Rightarrow 9 \times \frac{139}{139 + 200} = 3.69 \text{ V}$$

$$V_o = 2.94 \times 3.69 - 9.29 = 1.5586 \text{ V} \# \text{ , Digital O/P} = 133$$

في حالة قياس الضغط في الماء في عمق 100 متر في البحر المتوسط

$\textcircled{Q2}$ $S = 0.14 \text{ mA/g}$, $@ 0g = 7 \text{ mA}$ ($\pm 30g$) , VFC (4V/6KHz)

\textcircled{B} $(-30 \times 0.14) + 7 = 2.8 \text{ mA}$, $(30 \times 0.14) + 7 = 11.2 \text{ mA}$, $(2.8 \sim 11.2 \text{ mA})$

$$R = 100 \Omega \rightarrow (0.28 \text{ V} \sim 1.12 \text{ V})$$


$$\frac{1}{4/6} \frac{\text{KHz}}{\text{V}} \rightarrow (0.42 \text{ KHz} \sim 1.68 \text{ KHz})$$

$$T = 0.2 \text{ sec} \rightarrow (84 \sim 336 \text{ Pulse}) \rightarrow (01010100, 10101000)_2$$

\textcircled{C} $(-0.5g) \rightarrow (-0.5 \times 0.14) + 7 = 6.93 \text{ mA}$ $\times 100 \Omega = 0.693 \text{ V}$

$$\rightarrow 1.0395 \text{ KHz} \times 0.2 \text{ sec} = 208 \text{ Pulse} \rightarrow (11010000)_2$$

$\textcircled{Q3}$

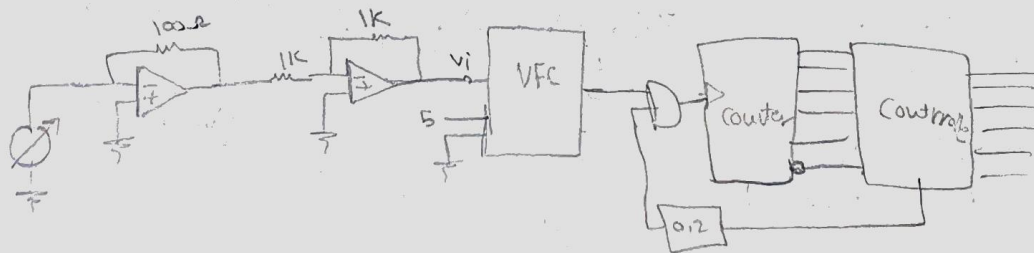


$\textcircled{Q3}$ $S = 5 \text{ mV/bar}$, $5 \Omega/\text{cm}$ PoT , 150 cm

$(V_s = 9 \text{ V} , R_i = 150 \Omega)$ Green $L > 70 \text{ cm}$
 $P < 5 \text{ bar}$

ref \swarrow min 0.09 d
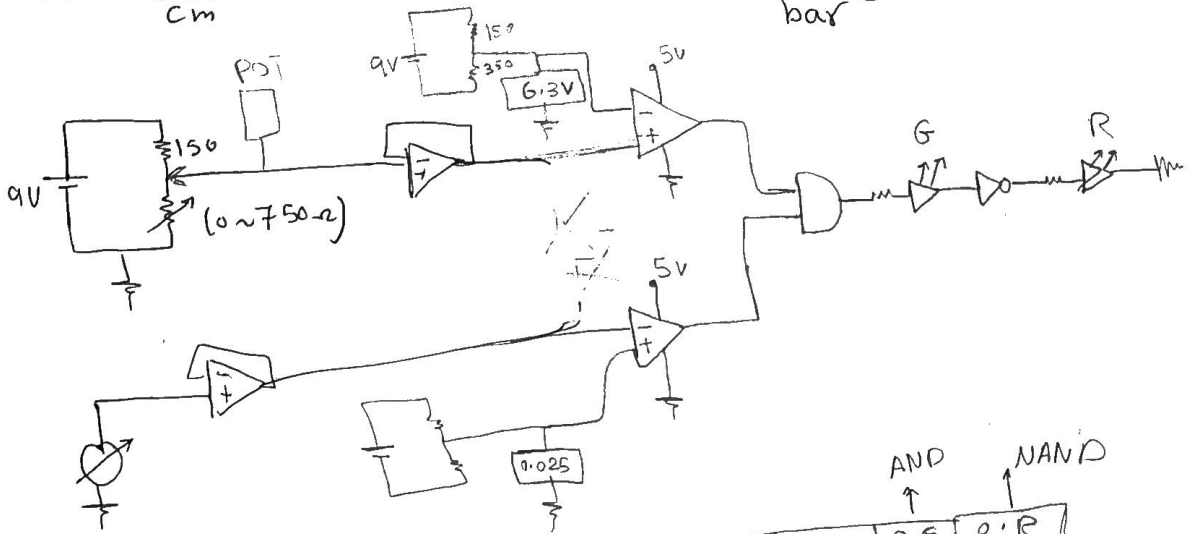
$$150 \times \frac{5\Omega}{cm} = 750\Omega, \quad 5bar \times \frac{5\frac{mV}{bar}}{bar} = 25mV$$



A hand-drawn truth table for AND and NAND gates. The table has four columns: A, B, O.F (Output of AND), and O.R (Output of NAND). Above the table, 'AND' is written with an arrow pointing to the O.F column, and 'NAND' is written with an arrow pointing to the O.R column. The rows represent the four possible combinations of inputs A and B (0, 0; 0, 1; 1, 0; 1, 1). The O.F column contains the results of the AND operation (0, 0, 0, 1), and the O.R column contains the results of the NAND operation (X, 1, 1, 0).

A	B	O.F	O.R
0	0	0	X
0	1	0	1
1	0	0	1
1	1	1	0

قیم مش و اخذ $Q(14)$

Q(5) $V = 19 \text{ mV}$ $T = ?$, $T = -40^\circ$ $V = ?$ $K\text{-Type}$
 $V = -1.50 \text{ mV}$ #

$$V_L = 18.94, V_H = 19.15$$

$$T_L = 460, T_H = 465$$

$$L = 460, TM = 465$$

$$V_m = V_L + \left(\frac{T_M - V_L}{T_M - T_L} \right) (T_m - T_L) \Rightarrow 19 = 18.94 + \left(\frac{19.15 - 18.94}{5} \right) (T_m - 46)$$

$$T_m = 461.43^\circ$$

Final Spring 2018 (30~120°C), VFC (2V/1KHZ)

Final Spring 2018

Q(2) $S = 5 \text{ mV}/^\circ\text{C}$, $(30 \sim 120^\circ\text{C})$, $V_{FC} (2 \text{ V}/1 \text{ KHz})$

$(2 \sim 5) \rightarrow (0.15 \sim 0.6 \text{ V})$

(2) $S = 5 \text{ mV}/^\circ\text{C}$
 sensor o/p Range $(30 \times 5 \sim 120 \times 5) \rightarrow (0.15 \sim 0.6 \text{ V})$
 $(75 \sim 300)$

VFC o/p Range $(0.15 \times \frac{1}{2/1} \sim 0.6 \times \frac{1}{2}) \rightarrow (75 \sim 300 \text{ Hz})$

Counte o/p Range $(75 \times \frac{1}{10} \sim 300 \times \frac{1}{10}) \rightarrow (7.5 \sim 30 \text{ pulse})$

$$T = 112^{\circ}\text{C} \rightarrow 112 \times 5 \frac{\text{mV}}{\text{C}} = 0.56 \text{ V} \rightarrow 0.56 \text{ V} \times 0.5 \frac{\text{kHz}}{\text{V}} = 0.28$$

$$280 \text{ Hz} \times \frac{1}{10} = 28 \text{ Sample } \#$$

$$Q(3) \quad S = 0.13 \text{ mA / bar} \quad , \quad (-20 \sim +20 \text{ g}) \quad , \quad @ \quad \bar{\theta} = 4 \text{ mA} \quad , \quad R = 150$$

ADC (8bit, $\pm 4\text{V}$ ref)

$$\text{Sensor o/p} \quad (-20 \times 0.13) + 4 \sim (20 \times 0.13) + 4 \Rightarrow (1.4 \sim 6.6 \text{ mA})$$

$$\Rightarrow (1.4 \times 150 \sim 6.6 \times 150) \approx (0.21 \sim 0.99 \text{ V}) \xrightarrow{\text{Digital o/p} \rightarrow} (135 \sim 160)$$

$$\Delta V = \frac{8}{2^8} = 0.03125 \quad \text{Digital o/p} = \frac{\text{analog I/P}}{0.03125}$$

$$\Delta (P = 8 \text{ bar}) \Rightarrow (8 \times 0.13) + 4 = 5.04 \text{ mA} \times 150 \Omega = 0.756 \text{ V}$$

$$\text{Digital o/p} = \frac{0.756 + 4}{0.03125} = \left(\frac{152}{10} \right) \rightarrow \begin{matrix} 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ 1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 \end{matrix}_2$$

$$\Delta (\text{Digital o/p} = 18H) \Rightarrow (18)_H = (00011000)_2 = (24)_{10}$$

$$\text{analog I/O} = (24 \times 0.03125) - 4 = -3.25 \text{ V OUT OF RANGE}$$

Q(4) " رقة في الورقة "

$$\text{DAC} = \begin{pmatrix} 0 & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \end{pmatrix}_2 \Rightarrow (85)_{10} \Rightarrow \text{analog I/P} (0.664)^{\text{volt}}$$

$$\Delta V = \frac{2}{2^8} = 7.8125 \times 10^{-3} \quad , \quad \text{Digital o/p} = \frac{\text{analog I/P}}{7.8125 \times 10^{-3}}$$

$$V_o = \left(\frac{R_f}{R} + 1 \right) V_i = \left(\frac{1.7}{1} + 1 \right) \times 0.664 = 1.7928 \text{ V } \#$$

$$\Delta V = \frac{5}{2^8} = 0.0195 \quad , \quad \text{Digital o/p} = \frac{1.7928}{0.0195} = (92)_{10}$$

$$(0101100)_2$$

(5) $R_{ref} = 40^\circ C$

$V = ?$ if $T = 120^\circ C$

J-Type

△

$$V_{J40}(120) = V_{J0}(120) - V_{J0}(40)$$

$$6.38 - 2.06 = 4.32 \text{ mV}$$

△

	①		②		
C°	0	5	10	15	20
R	107.6	109.1	110.2	111.7	113.7

$$T = 11.4^\circ C$$

$$R(T) = R(T_0) * (1 + \alpha_1 \Delta T + \alpha_2 \Delta T^2) \quad , \quad \alpha = \frac{1}{R(T_0)} \cdot \frac{R_2 - R_1}{T_2 - T_1}$$

Assume $R(T) = 111.7$

$$111.7 = 110.2 \times (1 + 1.86 \times 10^{-3} \times 10 + \alpha_2 \times 100)$$

$$\alpha = \frac{1}{110.2} \cdot \frac{111.7 - 107.6}{20}$$

$$\alpha_2 = -4.98 \times 10^{-5}$$

$$\alpha = 1.86 \times 10^{-3} \text{ } \#$$

$$T = 11.4^\circ C \rightarrow$$

$$R(T) = 110.2 \times (1 + 1.86 \times 10^{-3} \times (11.4 - 10) + 4.98 \times 10^{-5} (11.4 - 10)^2)$$

$$R(T) = 110.47^\circ C \text{ } \#$$

Final SPRING 2017

Q11) $S = 4 \Omega / ^\circ C$ ($\pm 25^\circ C$) @ $0^\circ C = 280 \Omega$, Wheatstone B/V
use Transm
(8bit, 0~5V) ADC

$$((-25 \times 4) + 280 \sim (25 \times 4) + 280) \rightsquigarrow (180 \Omega \sim 380 \Omega)$$

$$R_1 = 100, R_2 = 120, V_s = 9V$$

$$R_1 R_4 = R_2 R_3$$

$$100 \times 180 = 120 \times R_3 \rightarrow R_3 = 150 \Omega$$

$$V_a = 9 \times \frac{150}{150 + 100} = 5.4 \text{ V}, \quad V_{b1} = 9 \times \frac{180}{180 + 120} = 5.4 \text{ V}$$

$$V_{b2} = 9 \times \frac{380}{380 + 120} = 6.84 \text{ V} \rightsquigarrow (0 \sim 1.44 \text{ Volt})$$

$$V_o = V_i + 1 \quad \text{using Transm} \rightsquigarrow (1 \sim 2.44 \text{ Volt})$$

7

$$\Delta V = \frac{5}{2^8} = 0.0195$$

$$(51 \sim 125)_{10} \rightarrow \text{Digital O/P}$$

$$(00110011, 0111101)_2$$

$$\Delta T = -2^\circ\text{C} \rightarrow (-2 \times 4) + 280 = 272 \text{ }^\circ\text{C}$$

$$V_b = 9 \times \frac{272}{272 + 120} = 6.24 \rightarrow (6.24 - 5.4) = 0.844 \text{ V} + 1 = 1.844$$

$$\text{Digital O/P} = (94)_{10} \rightarrow (01011110)_2$$

$$Q(2) \quad S = 0.33 \text{ mA/g} \quad (\pm 20\text{g}) \quad \text{ADC (8bit, } \pm 4)$$

$$\text{Sensor O/P } (-20 \times 0.33) \sim (20 \times 0.33) \Rightarrow (-6.6 \sim 6.6 \text{ mA}) \quad \text{Assume } R = 100\Omega$$

$$(-0.66 \sim 0.66 \text{ V}) \quad \left[\text{need Transmitter } (0.34 \sim 1.66 \text{ V}) \right] \rightarrow \text{محول}$$

$$\Delta V = \frac{8}{2^8} = 0.03125, \quad (107 \sim 149)_{10} \rightarrow \text{Digital O/P}$$

$$\Delta (-3\text{g}) \rightarrow -3 \times 0.33 = -0.99 \text{ mA} \times 100 = -0.099 \text{ V}$$

$$\text{Digital O/P} \rightarrow (124)_{10} \rightarrow (01111100)_2$$

$$\Delta (0.6 \text{ H}) \rightarrow (00000110)_2 \rightarrow (6)_{10} \quad \text{OUT OF RANGE}$$

$$Q(3) \quad (10 \text{ bit } 10 \sim 5 \text{ V}) \text{ ADC, Sensor O/P } (\pm 150 \text{ mV})$$

$$F_s = 15 \text{ Hz}, \quad V_N = 20 \text{ mV}, \quad f_N = 150 \text{ MHz}, \quad \text{attenuate } (25\%)$$


$$\Delta V = \frac{5}{2^{10}} = 4.88 \times 10^{-3}$$

$$25\% = \frac{1}{\sqrt{1 + \left(\frac{150}{F_c}\right)^2}} \Rightarrow F_c = 38.72 \text{ Hz}$$

$$V_o/V_i = \frac{1}{\sqrt{1 + \left(\frac{15}{38.72}\right)^2}} = 0.9324 \sim 93.2\% \quad \text{Good}$$

$$\Delta V_{i0} (-150 \text{ mV} \sim 150 \text{ mV}) \xrightarrow{+20 \text{ mV}} (-0.13 \sim 0.17 \text{ V})$$

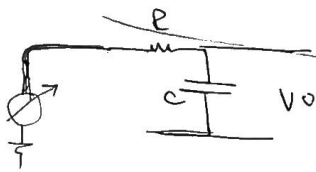effect of filter in sensor o/p $(-0.13 \times 0.9324) \sim (0.17 \times 0.9324)$
 $(-0.12 \sim 0.16 \text{ V}) \#$



$$V_o = V_i + 1 \rightarrow (0.88 \sim 1.16 \text{ V})$$

Digital o/p $(180 \sim 237)_{10}$

$$(00010100, 0011101101)_2$$

Q(u) Type-J

a) $T = 32^\circ \text{C}$ $V = ?$

b) $T > 32^\circ \text{C} \rightarrow \text{ON Cooler}$


$$\Delta T_L = 30, V_L = 1.54$$

$$T_H = 35, V_H = 1.8$$

$$T_m = T_L + \left(\frac{T_H - T_L}{V_H - V_L} \right) (V_m - V_L)$$

$$32 = 30 + \left(\frac{5}{0.26} \right) (V_m - 1.54)$$

$$V_m = 1.644 \#$$

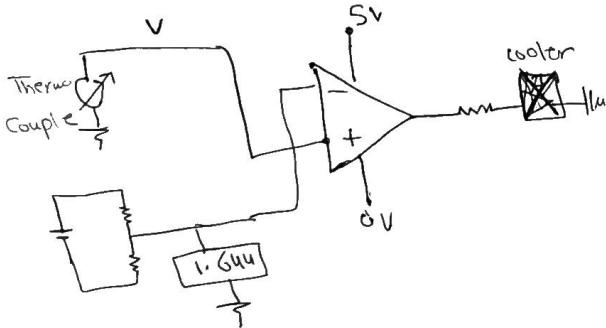

c) $T = 13^\circ \text{C} \rightarrow R = ?$, $T < 13 \rightarrow \text{ON heater}$

	1	0	2		
$^{\circ}\text{C}$	0	5	10	15	20
Ω	107.6	109.1	110.2	111.3	111.7

$$\alpha = \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1} = 1.86 \times 10^{-3}$$


$$R(T) = R(T_0) (1 + \alpha \Delta T)$$

$$R(T) = 110.2 (1 + 1.86 \times 10^{-3} \times 3)$$

$$R(T) = 110.8 \Omega \#$$

$$V = 9 \times \frac{110.8}{110.8 + 120} = 4.32 \text{ V} \#$$

Assume $R = 120\Omega$, $V_s = 9V$

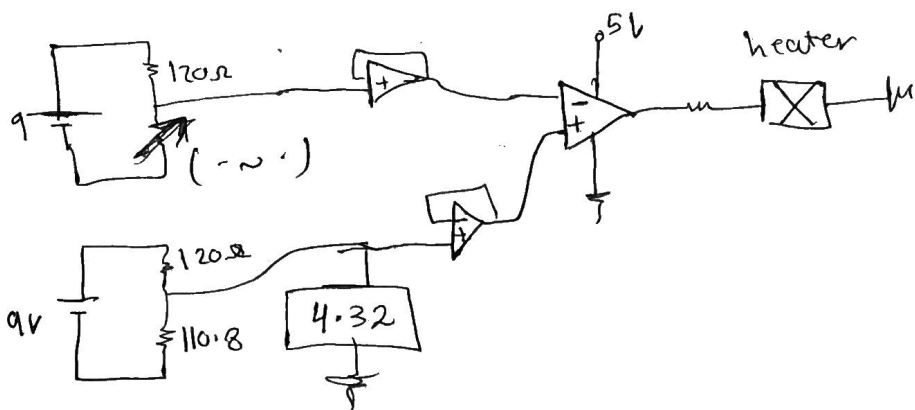

Q(13) S-19 Final

$$\Delta (0.456 \text{ V} \sim 1.52 \text{ V})$$

$$-4 = 0.456M + F$$

$$4 = 1.52M + F$$

$$8 = 1.064M$$

$$M = 7.518$$

$$F = -7.428$$

$$V_0 = 7.518 \text{ V}; -7.428$$

$$\left[\begin{matrix} (-4 \sim 4 \text{ V}) \\ (0 \sim 256)_{10} \end{matrix} \right]_{10}$$

$$\Delta (89 \times 0.14) + 5.2 = 6.32 \text{ mA} \times 190 \Omega = 1.2 \text{ V} \rightarrow 1.5936 \text{ V}$$

$$\text{Digital o/p} \approx (\cancel{178})_{10} \rightarrow (1011000)_2$$

$$\Delta \text{ oD} \rightarrow 13, 92 \rightarrow 146$$

$$D_0 \times \Delta V = -3.59, 0.5625$$

$$V_0 = V_i M + F = 0.51 \text{ V}, 1.6628 \text{ V}$$

$$V/R = I = 2.68 \text{ mA}, 5.59 \text{ mA}$$

$$g = -18 \text{ g}, 2.79 \text{ g}$$

Q(13) S-18 Final

$$(0.21 \sim 0.99) \text{ V},$$

$$-4 = 0.21M + F$$

$$4 = 0.99M + F$$

$$8 = 0.78M$$

$$M = 10.25$$

$$F = -6.65$$

$$V_0 = 10.25 \text{ V}; -6.65$$

$$\Delta (8 \times 0.13) + 4 = 5.04 \text{ mA} \times 150 \Omega = 0.756 \text{ V} \rightarrow \cancel{2.2} \text{ V} \rightarrow 1.599$$

$$(179)_{10} \rightarrow (10110011)_2$$

$$\Delta (18)_H \rightarrow (24)_{10} \rightarrow -3.25 \text{ V} \rightarrow 0.28 \text{ V} \rightarrow 1.88 \text{ mA}$$

$$(-16.25)_9$$